



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Automotive](#) > APP 735

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [General Engineering Topics](#) > APP 735

[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Tutorials](#) > [Power-Supply Circuits](#) > APP 735

Keywords: printed circuit board, PCB layout, parasitic inductance, parasitic capacitance, EMI, DC-DC, dc dc, converters, convertors, ground plane, ground loop

TUTORIAL 735

Layout Considerations for Non-Isolated DC-DC Converters

Nov 29, 2001

Abstract: DC-DC converters are an excellent source of electric fields and magnetic fields. Their EMI spectrum begins at the switching frequency and often extends over 100MHz. To minimize capacitive couplings and magnetic couplings care must be exercised in printed circuit board (PCB) layout. Parasitic capacitance and parasitic inductance of the circuit must be evaluated so that the proper trade-off can be made early in the design phase.

For many years, repeated introductions of integrated DC-DC power-supply controllers have given us ever-higher levels of performance. These ICs unburden the systems engineer by removing the task of power-supply design, but this simplification has led to a loss of knowledge. Switching converters should therefore serve as a reminder to be careful. The following discussion presents rules for avoiding surprises when designing board layouts for non-isolated DC-DC converters.

The first rule in optimizing such a layout is to *isolate the converter*. DC-DC converters are an excellent source of electric and magnetic fields. Their EMI spectrum begins at the switching frequency and often extends over 100MHz. To minimize capacitive couplings and "magnetic-field-to-loop" couplings, you should locate the converter away from other circuitry, especially from low-level analog circuitry.

Isolating the converter is not always easy. Some boards accept input voltage on one side of the converter and distribute output voltages on the other side. VME cards or telecom cards, for example, include very complex routings with currents as high as 20A. A single connector brings in the input voltage and distributes several output voltages to the backplane. Therefore, there's a strong temptation to place the converter near this connector to reduce resistive drop. The area, however, is dense with interface drivers, backplane buses, and so forth, with the associated risk of noise coupling. A power connector can be added in some cases, but that solution entails extra board area and cost.

Resistance in the copper traces is the most constraining factor. For a trace of a given length and thickness, this resistance is

$$R = \rho \times (l/S)$$

where l is the trace length in meters, S is the trace area in square meters, and ρ (the resistivity of copper) is $1.7 \times 10^{-8} \Omega \cdot m$ at $20^\circ C$, or $2.1 \times 10^{-8} \Omega \cdot m$ at $70^\circ C$. As an example, the resistance of a copper trace 0.5cm wide and $35 \mu m$ thick at $20^\circ C$ is $1 m\Omega/cm$. That value may appear negligible, but it

- C6 and V_{dd}
- C6 and Q2(S)
- C7 and BST, and C7 and LX
- Q1(G) and DH
- Q2(G) and DL
- Q1(S) and LX
- Q2(S) and PGND

Keep in mind that the parasitic inductance for a 1cm trace is about 10nH.

Looking closely at C6, you can see that it supplies Q1 and Q2, but not in the same way. It acts as a filter capacitor for Q1 and as a tank capacitor for Q2. Because we cannot place C6 near the high-side and low-side drivers at the same time, we place it as close as possible to V_{dd} and PGND (where the peak currents flow), and also near C7 (almost average current). Notice that the PGND, DL, and V_{dd} pins are side by side, and not by chance! Q2 and C6 are placed to minimize the ground-trace lengths between PGND, C6(-), and Q2(S). Connect this ground trace to the ground plane at a single point, near the PGND pin. To avoid common-impedance coupling, LX should be connected to Q1, and PGND/C6(-) to the source of Q2. **Figure 3** highlights the current paths during turn-off.

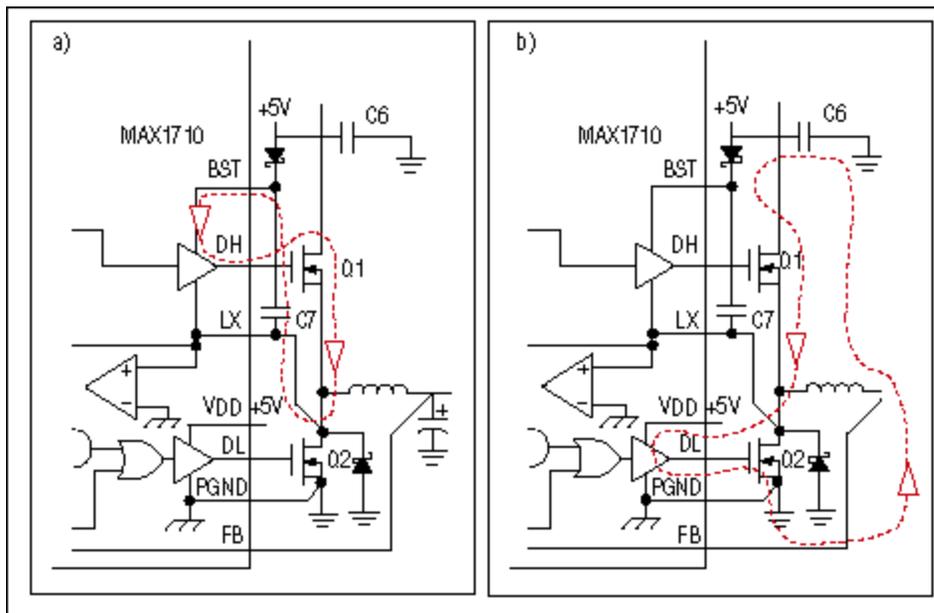


Figure 2. The dotted lines indicate heavy current flow in the gate-drive circuits for Q1 (a) and Q2 (b).

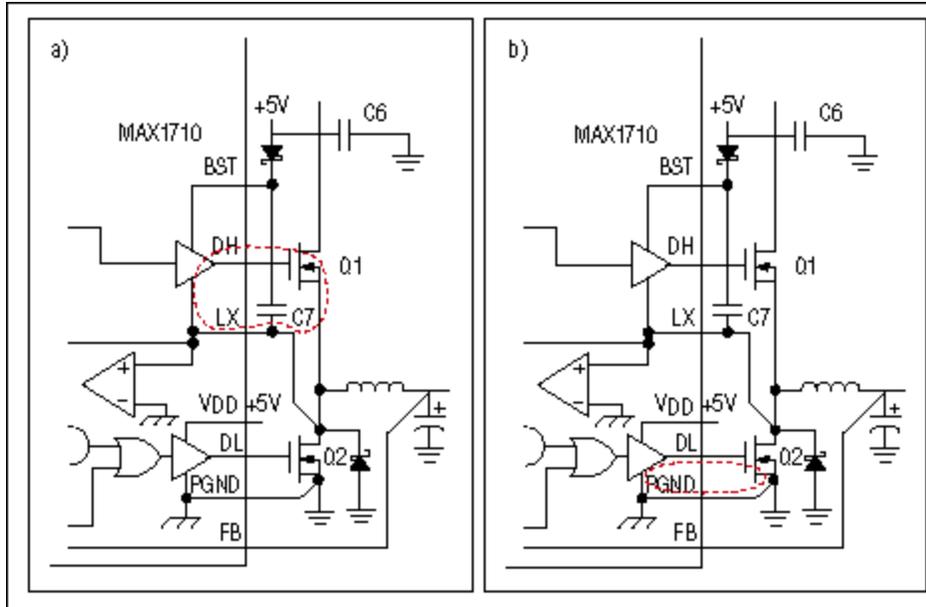


Figure 3. The dotted lines indicate heavy current flow in the gate-discharge (turn-off) paths for Q1 (a) and Q2 (b).

The number of "via" should be limited as much as possible. Indeed, the few tens of nanohenries added by a via is embarrassing when di/dt is high. For that reason, you should place all power components on the component layer, even the SMD ones. If you have no other choice, put several via in parallel.

We must remember that controllers are often oversized for the application at hand. Common practice, for instance, employs a 10A controller to produce a 3A output. Because we generally choose minimum-sized MOSFETs for cost reasons, the on-chip drivers remain oversized and therefore capable of more gate drive than is necessary.

Because the earlier discussion sought to avoid slowing the MOS gate drive, it seems paradoxical to place a small (10Ω to 100Ω) resistor in series with the gate drive. Oversized and/or fast drive waveforms, however, produce more switching noise and RF interference. At the other extreme, slow waveforms produce more switching loss in the MOSFET(s) and diode (if any). A good compromise is to reduce EMI by slowing the waveform slopes as much as possible, while maintaining an acceptable level of efficiency. (Components in the gate drive of **Figure 4b** let you trim the rise and fall times separately.) Fortunately, large drivers allow a final bit of optimization.

Routing the Power Stage

Figure 4 illustrates the two high-current loops common to many power converters. In responding to the perturbations caused by switching, these loops support high di/dt , and (at some nodes) high dv/dt as well. Identifying these loops helps to reduce their effects. Note that di/dt is great within the converter (at the switching node) but small outside the converter. Indeed, currents before the input capacitor and after the output capacitor reach a high value, but they are nearly continuous. Their AC components are low when the converter is well designed.

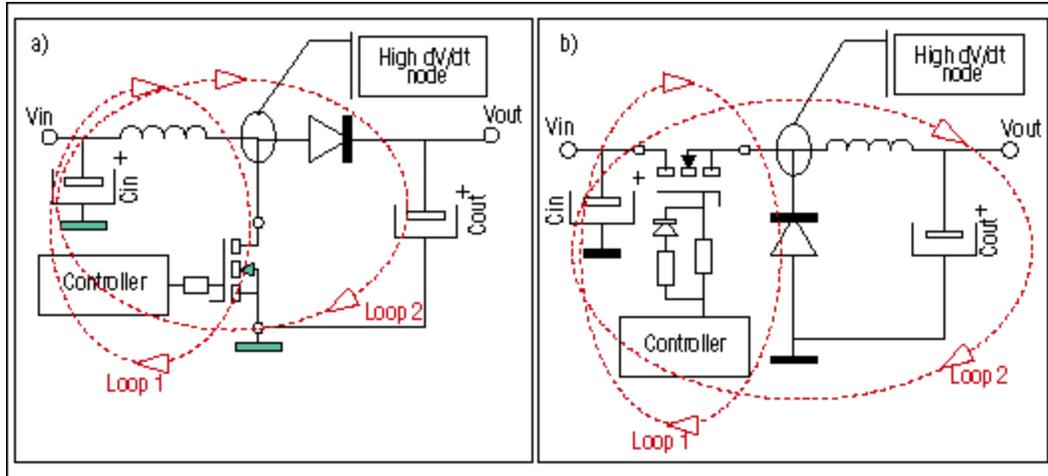


Figure 4. These simple schematics illustrate the basic operation of the step-up (a) and step-down (b) switching converters.

First, minimize parasitic inductance. We will consider a step-up converter, but the reasoning can be transposed for a step-down type. Figure 5 illustrates the kinds of parasitic inductance that cause the most problems.

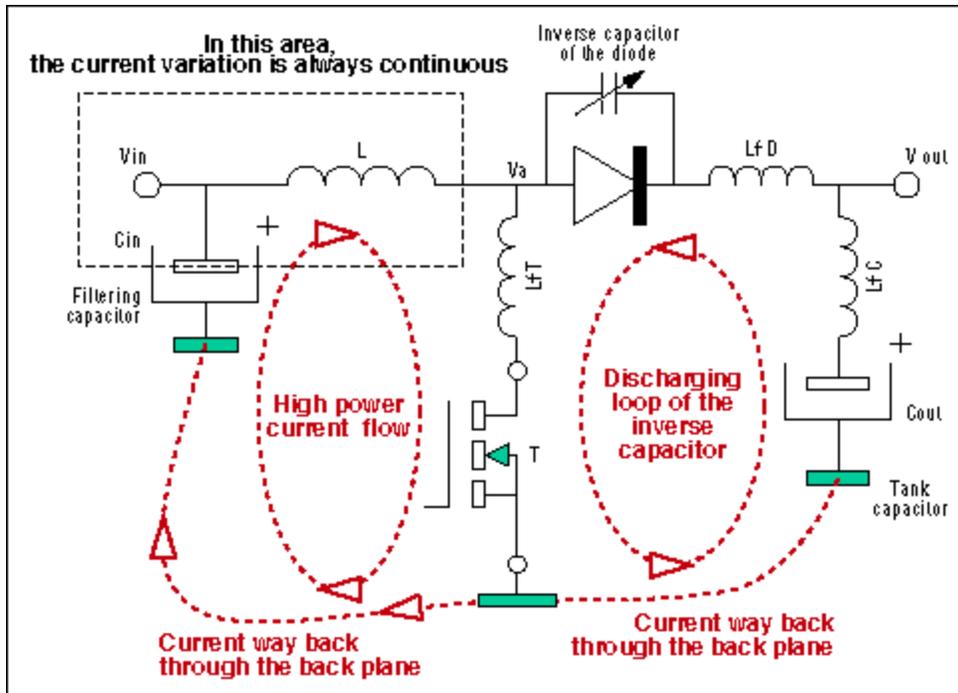


Figure 5. When the main switching transistor (T) turns off, the diode capacitance discharges as shown.

Without describing the 10 phases of a switching cycle, we can consider the MOSFET turn-off, when inductor current has been short-circuited by the MOSFET. The diode's inverse capacitor charges extremely fast via loop two, and the node-voltage V_a at the diode's anode (normally at $V_{out} - V_d$) goes to near 0V. The serial inductors ($L_{fT} + L_{fD} + L_{fC}$) increase this discharge time, thereby increasing switching loss in the MOSFET. These types of inductance also generate noise.

Peak current is limited by the transistor, which operates as a current source (V_{ds} still equals a few volts). For a 2A MOSFET, this current source could be 10A! The current level is large for a very short time (a few 10ns). Remember that varying the current through an inductor produces a voltage proportional to the current variation:

$$v = L \times [di(t)/dt]$$

This transition phase is a good spike generator! Once more, we minimize parasitic inductance by minimizing trace lengths and using short, wide traces around the MOSFET, diode, and C_{out} . You can now see how noise can be reduced by the control of slopes in the gate-drive waveforms.

To limit resistive voltage drops and the number of via, power-stage SMD components should be placed on the component side of the board and power traces routed on its component layer. If possible, the power ground should also be routed on the same layer. This arrangement has another benefit: less perturbation of the ground plane. To cancel radiated fields, take care to minimize the area of the power-current loop.

When it becomes necessary to route a power trace on a layer other than the component layer, choose a trace from the inductor or filter capacitors (i.e., C_{out} for a step-down converter, or C_{in} for a step-up converter). Because current through such traces is nearly continuous, it produces no noise, just a resistive drop. Parasitic inductance will be smaller if you route this trace on the layer just under the component layer. To avoid coupling by common impedance, you should separate PGND, the power-circuit ground, and the general ground plane (**Figure 6**).

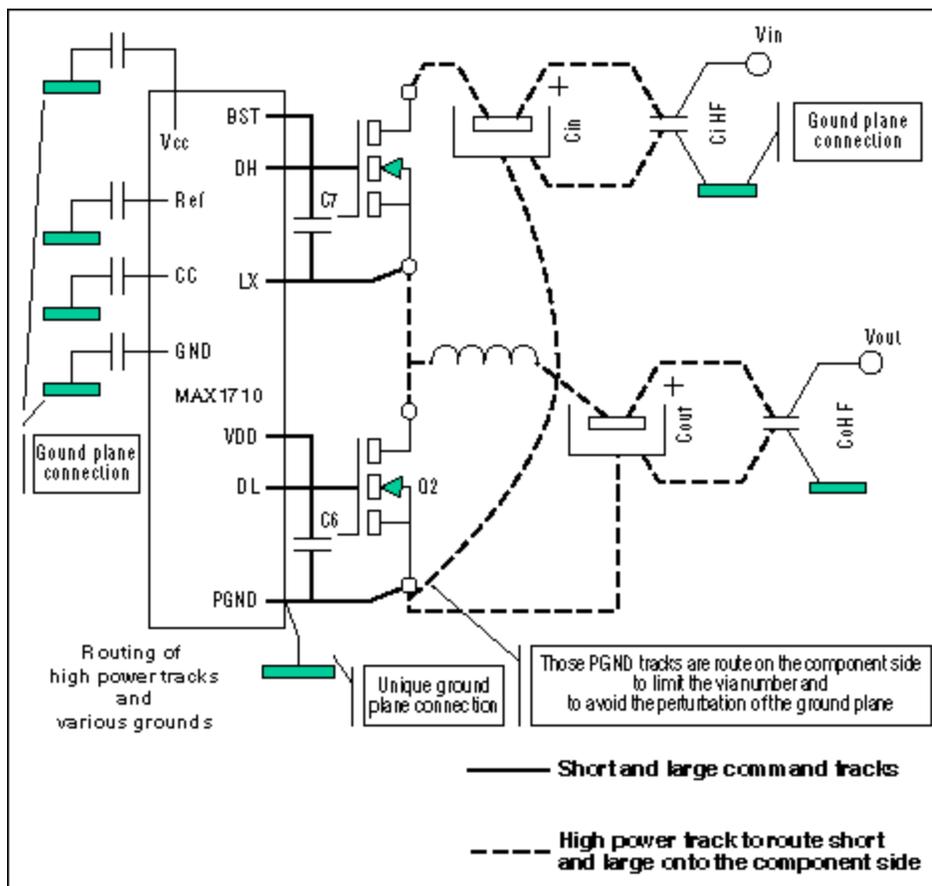


Figure 6. These details illustrate the routing of PGND versus gate-control traces in the controller circuit.

Capacitors and Other Components

It's important to pay close attention to the routing of traces from capacitor terminals in a DC-DC converter circuit. Large-valued low-ESR capacitors are expensive, and bad routings can cancel their performance. A good routing, on the other hand, can lower the output noise from 150mV to 50mV!

Ripple is directly related to the inductor value, the capacitor ESR, the switching frequency, and so forth, but HF noise (spikes) depend on parasitic elements and the switching action. We can anticipate spiking frequencies from 1MHz to 10MHz, depending on the switching frequency.

In a bad routing (**Figure 7a**), parasitic inductance associated with trace lengths causes trouble: L1 brings about an increase in noise, and L2 limits the attenuation of HF capacitor CoHF. The fix (**Figure 7b**) is to bring the input trace *in* on one side of the capacitor pad, and the output trace *out* on the other side of the pad.

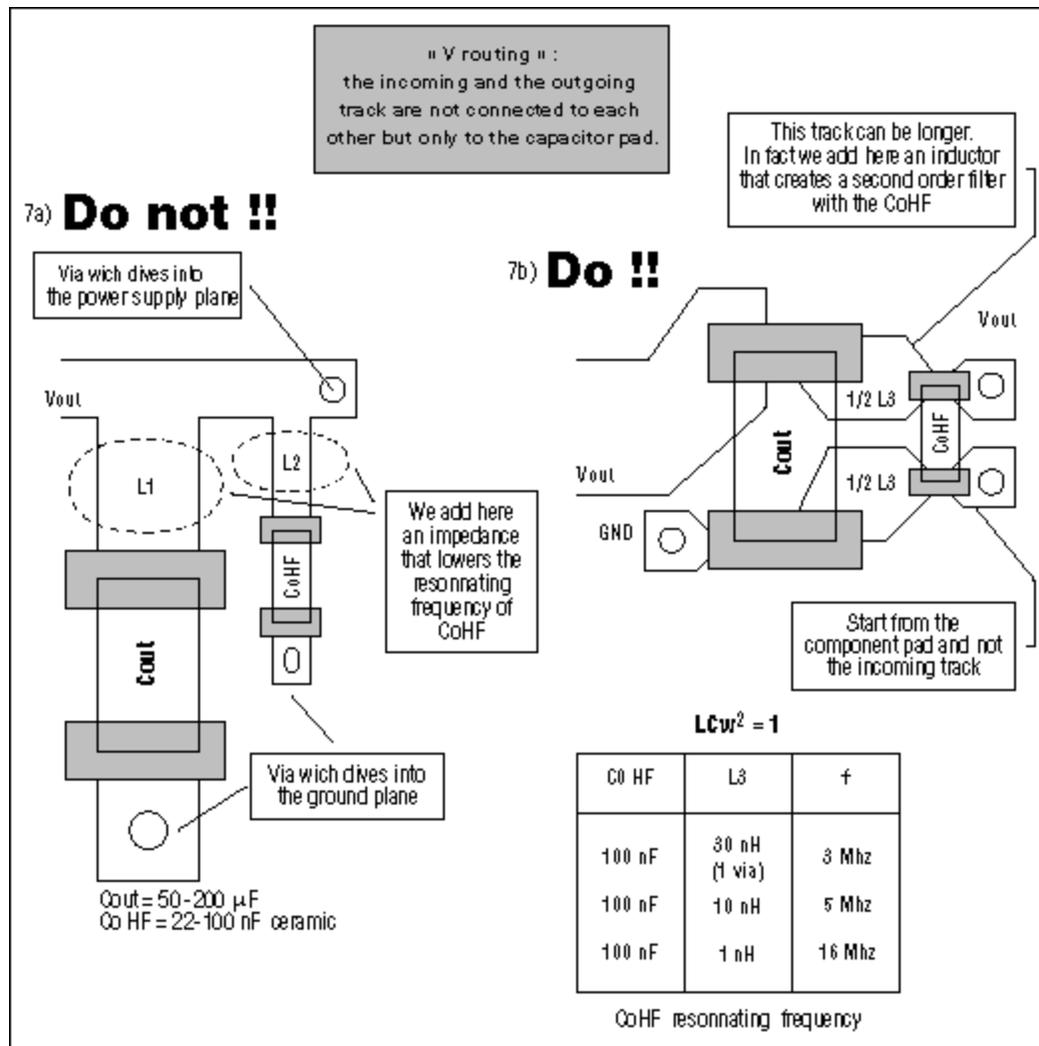


Figure 7. Improper routing of capacitor traces introduces unwanted parasitic inductance.

Now, having placed and routed the bulkiest parts, we turn our attention to the inductor. A deliberate but

unwanted coupling (**Figure 8a**) allows current in the power loop to pollute the controller supply (V_{cc}). High di/dt produced by switching through L_{p1} causes V_{cc} overshoots that easily reach several hundred millivolts. Using

$$v(t) = L \times [di(t)/dt]$$

with $L = 10\text{nH}$, $\Delta I = 1\text{A}$, and $\Delta t = 50\text{ns}$, $\Delta V = 0.2\text{V}$!

As mentioned earlier, the first precaution is to separate the power traces and be careful with PGND. The second precaution is to avoid connecting traces to the power loop (see **Figure 8b**). Traces that distribute the input voltage should be connected before the input capacitor and the controller's V_{cc} connection. Output voltage is distributed after the connections to the HF output capacitor.

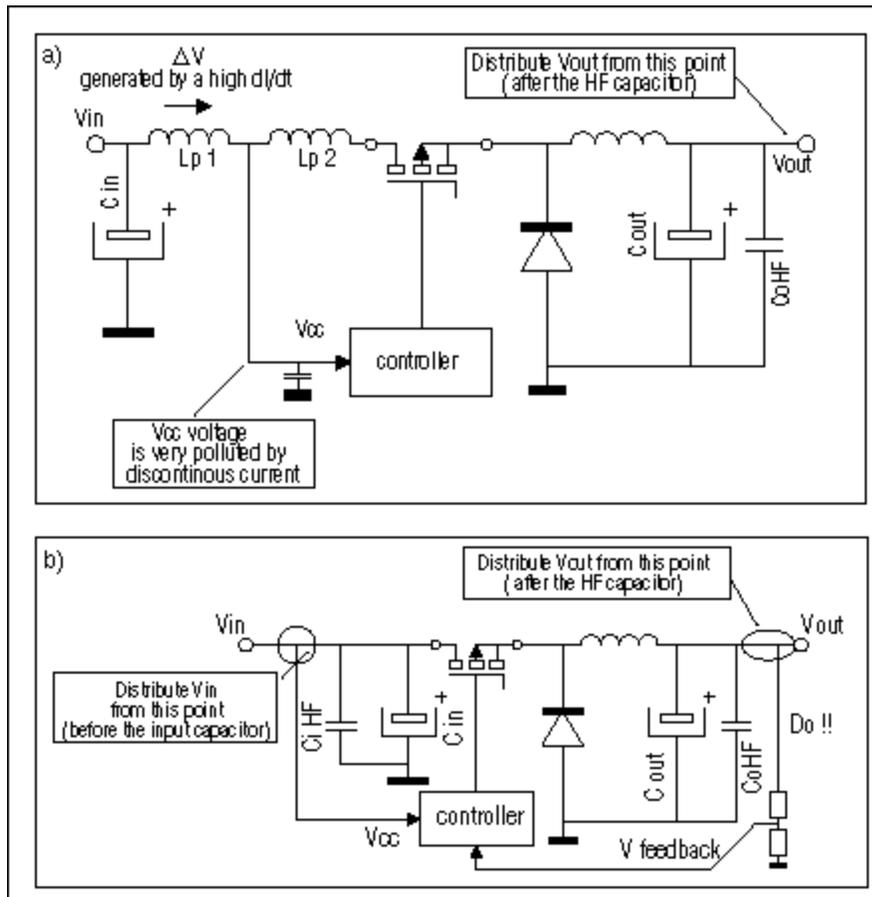


Figure 8. Unwanted common-impedance coupling (a) is prevented by the connections shown in (b).

Finally, some miscellaneous advice: Bad routing of the PGND trace can cause common-impedance coupling (one reason for the PGND terminal is to avoid polluting the controller's internal ground node). Move high-impedance traces (especially the output resistor divider that adjusts the output voltage) away from nodes that support high dV/dt . Currents induced by such coupling can make the controller oscillate.

MAX1710	High-Speed, Digitally Adjusted Step-Down Controllers for Notebook CPUs	
MAX1711	High-Speed, Digitally Adjusted Step-Down Controllers for Notebook CPUs	Free Samples
MAX1712	High-Speed, Digitally Adjusted Step-Down Controllers for Notebook CPUs	
MAX1846	High-Efficiency, Current-Mode, Inverting PWM Controller	Free Samples
MAX1847	High-Efficiency, Current-Mode, Inverting PWM Controller	Free Samples
MAX1864	xDSL/Cable Modem Triple/Quintuple Output Power Supplies	Free Samples
MAX1865	xDSL/Cable Modem Triple/Quintuple Output Power Supplies	Free Samples
MAX1865	xDSL/Cable Modem Triple/Quintuple Output Power Supplies	Free Samples
MAX1917	Tracking, Sinking and Sourcing, Synchronous Buck Controller for DDR Memory and Termination Supplies	Free Samples
MAX668	1.8V to 28V Input, PWM Step-Up Controllers in μ MAX	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 735: <http://www.maximintegrated.com/an735>

TUTORIAL 735, AN735, AN 735, APP735, Appnote735, Appnote 735

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>